

Construction project:

FLEXIBLE COUNTER MODULE

If you've ever wanted to fit a digital readout to your latest project, or needed a flexible counter module that could be easily expanded and modified to suit, then this little project should fit the bill nicely. Using a simple 'sandwich' technique, this counter module takes up a minimum of space on the front panel, and you can extend the count to as many digits as you like by simply adding extra units.

by GRAHAM CATTLEY

It's been quite a while since we've presented a general purpose counter unit, and looking back at past designs we realised that there wasn't really anything that offered a degree of flexibility in the number of digits, while also providing an aesthetically pleasing display. Most designs provide three digits, but if you wanted to add more, there was no way to link on the next unit and still maintain an equal spacing between each of the displays.

To make matters worse, supplies of the much-loved 74C926 counter and seven-segment driver IC that was used in a lot of earlier designs have dried up, leaving many previous designs now unbuildable. All of this highlighted the need for a flexible counter module that was small and expandable, but still offered a goodly number of control inputs to make it easy to adapt to new and existing designs.

Features

With this new design, each digit is completely independent of any other digit, and so the modules can be cascaded to give anything from three to 30 digits, and can even be cut down to give two digits (or even one) if required.


Each digit has a full complement of control inputs, including lamp test, blanking, output latching, up/down counting, input gating, reset and clock. As well, the design uses standard CMOS, and so will run off a wide range of supply voltages.

With minimal additional circuitry the counter could be expanded to count up to millions of events, or with a suitable front end and gating circuit it could be the basis of a simple frequency meter.

The circuit

As you can see from the schematic, the circuitry behind each of the three digits is identical, and so I'll just cover the operation of the first digit here, based around IC1 and IC2.

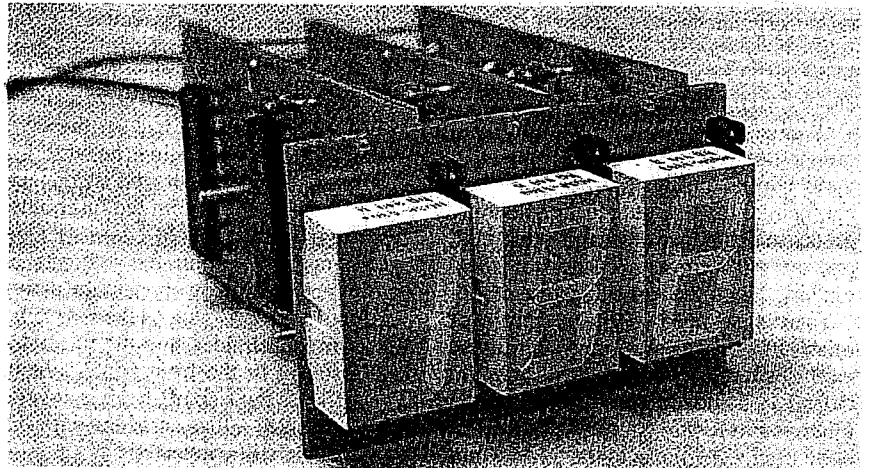Most of the work in this circuit is done by the 4029 counter IC. This IC is very flexible, and can be configured to count in a number of different modes by tying



Although a little unconventional in design, this counter module can be easily expanded to as many digits as required. A full range of control inputs is available as well, making this module suitable for use in existing designs.

the relevant control pins high or low. IC1 drives the right hand (least significant) digit on the display, and clocks on a rising edge from whatever circuitry is driving the counter. If the counter is to be clocked mechanically (a switch contact or pressure mat for example) the incoming signal driving the counter should be suitably de-bounced, and its peak voltage should be clamped so that it doesn't exceed the counter's supply rails.

IC1's output is a four-bit binary word, which (depending on the configuration) will count to a maximum of 15 before resetting back to zero.

In this application we only want it to count up to nine before resetting, and so the counter's BIN/DEC input (pin 9) is held permanently low, selecting a decimal rather than binary counting mode.

The BCD output feeds into IC2, a 4511 BCD to seven segment decoder driver IC, which decodes the four bit word and outputs the correct display code for each count. Resistors R6 to R13 limit the current to each segment to around 20mA, which gives a nice bright display.

Both IC1 and IC2 support a total of five control inputs, and these are all held in their inactive or 'normal' states by the five 10k resistors R1 to R5. The follow-

ing list describes the function and effect of each of these inputs.

• Up/Down

High — counts up from 000;
Low — counts down from 000.

• Latch

High — freezes the display only, with the counter still enabled;
Low — display updated with each count.

• Blank

High — digit turned on;
Low — digit turned off, counter still enabled.

• Lamp test

High — no effect;
Low — all segments of digit turned on, counter still enabled.

• Gate

High — counter enabled;
Low — counter stopped.

As well as the five inputs listed above, each digit has a clock and reset input as well as a carry-out output. Carry-out is connected to IC1's TC (Terminal Count) pin, which pulses low every time the counter reaches nine (when counting up) or zero (when counting down). This output is used to clock the next counter in the module (here shown as IC3) and acts as a

Flexible Counter Module

to the following (unoccupied) pads: Up/down, Latch, Lamp Test, V+, Reset, Gate and Ground.

If your application is going to support leading zero blanking, it would be a good idea to attach leads to the 'Blank' pin on each board now, as it's a little difficult getting to this pin once all the boards have been soldered together.

With the tinned copper wires poking up from the bottom of the first logic board, position the nine copper fingers along one edge of the board so that they line up with the nine pins belonging to the left hand digit of the display board.

Just tack solder a couple of the pins, and then check that the two boards are correctly aligned, and are sitting at 90° to each other. Also double check that you have actually connected it to the left hand (most significant) digit, otherwise you'll find it rather difficult to solder in the remaining two boards...

Testing, testing



If all's well, you can fully solder all the pins, and the first digit should be complete. As a test, try applying power to the logic board and checking that it lights up correctly, and counts at around 50Hz if the clock input is touched with a wet finger (you can, of course, use a signal generator instead, but wet fingers are usually closer to hand, so to speak).

With the left-hand digit working, you can now mount the second logic board to drive the middle digit. Carefully thread the board over the tinned copper wires, making sure that each wire goes through the correct hole — some holes are unused on the second and third boards, so it pays to be careful.


Position the fingers with the pins as before, and again check that everything is at right angles before soldering it in place permanently.

Check again that this second digit counts in the same way as the first, and then link this second board's carry-out pad to the first board's clock pad with a short length of tinned copper wire. You

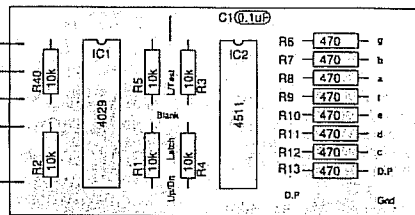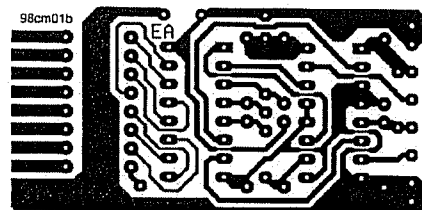Full sized artwork for both boards. You will need one logic board (below) for each digit in the display, making a total of four boards per module.



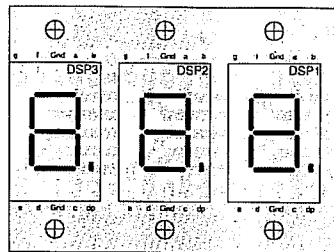Component overlays for both the logic board (above) and the display board at bottom.



PARTS LIST

Resistors

R1-R5, R40 10k
R6-R13, R19-R25, R32-R39
470 ohms (see text)

Capacitors

C1-C3 0.1uF monolithic

Semiconductors


IC1,3,5 4029 CMOS BCD counter
IC2,4,6 4511 CMOS 7-segment
decoder/ driver
DSP1,2,3 FND500/5303 or equiv. 13mm
common cathode display

Miscellaneous

PCBs — 1 x 98cm01a (46 x 28mm), 3 x
98cm01b (56 x 28mm); 1 x 28-way SIL head-
er strip; 9 x PC pins; 400mm tinned copper
wire; hookup wire, solder etc.

should now find that you can clock the middle digit at 50Hz as before, and the first digit will clock at a tenth of the speed (5Hz). It's a good idea to follow this check-as-you-go procedure, as finding faults after all the boards have been wired together can get a bit fiddly.

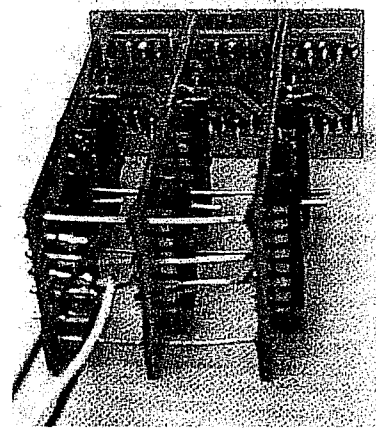The last board is connected in the same way as the second; this one should have the extra PC pins on it, and once it has been connected to the display board and the feed throughs soldered in you



This shot shows how feed through links are used to connect between boards. All off-board connections are made to the board driving the right hand digit.

can then connect its carry out to the clock input on the middle board.

All three digits should now light up when power is applied, and they should count from 000 to 999, with the last (left) digit incrementing every 0.5Hz, or once every two seconds.


Extra digits

If you want to extend the counter to give four, five six or more displays, then it is a simple matter to repeat the above procedure for as many digits as you want. You can trim off any excess display board and mount the extra module(s) to the right of the original displays. You may find it easier to construct and test each module as a separate unit, and then wire them together with hookup wire, rather than trying to construct a 'mini skyscraper' on the bench...

Only one set of pull up/down 10k resistors will be needed no matter how many digits you have, so it's probably best to leave them on the first module and omit them from all the others.

To make it easier to physically align more than one display board, the top and bottom edges of each of the display boards have a wide copper track running along them. This track can be used to hold a 10mm long piece of stout wire soldered between the two adjoining display boards, which will keep them lined up.

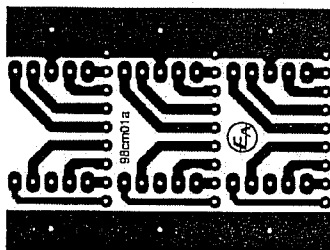To mount the display in your case, you are probably best off enlarging the mounting holes on the top and bottom of the display board to accept some M3 x 15mm countersunk screws. You can then use four 10mm spacers to mount the module behind a rectangular cutout in the front panel, covered with clear red perspex or other suitable filter material. ♦



Construction Notes


K 2505 3 Digit Counter Module Kit

Dear Customer

We have introduced a small modification to the input circuitry for the K 2505 to enable it to better cope with inputs that are not CMOS in nature. The circuit is a form of "limiter" which will protect the 4029 IC from damage to it's CLOCK input.

The modified schematic is shown below, and the components may be soldered underneath the PCB, on the copper side of the board.

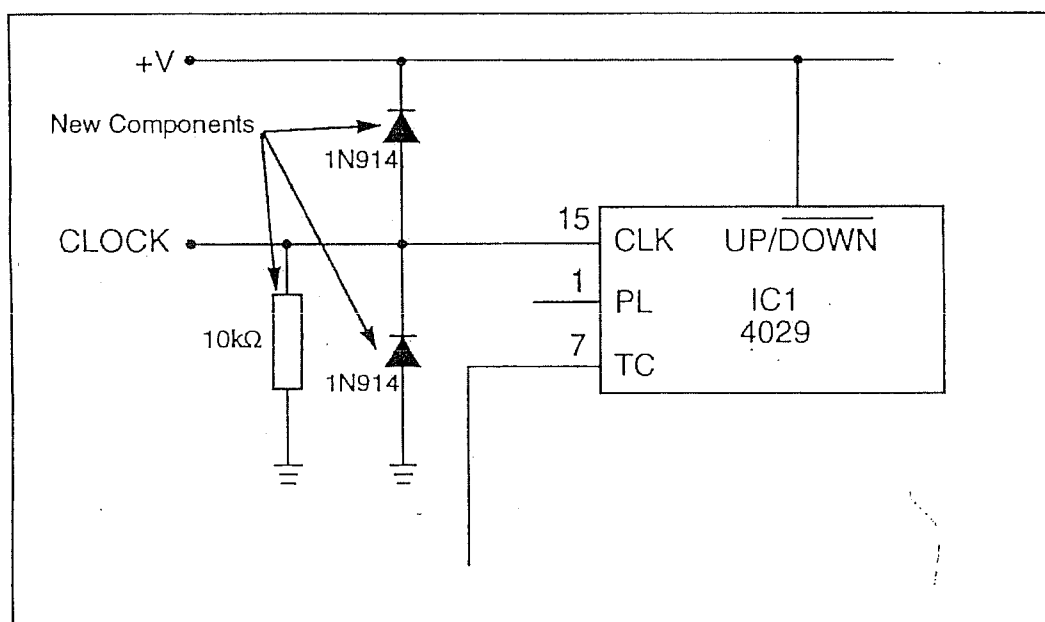We have included the components for this modification at no extra cost.



Happy Constructing!

Kit Department